
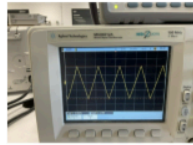


LT6221

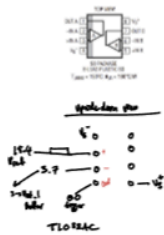


Ideas

- Differential measurement to reject supply, temp & drift

Hysteresis 0.5V - 2.5V → What happens if you reduce this?
↳ Use decoupling capacitors

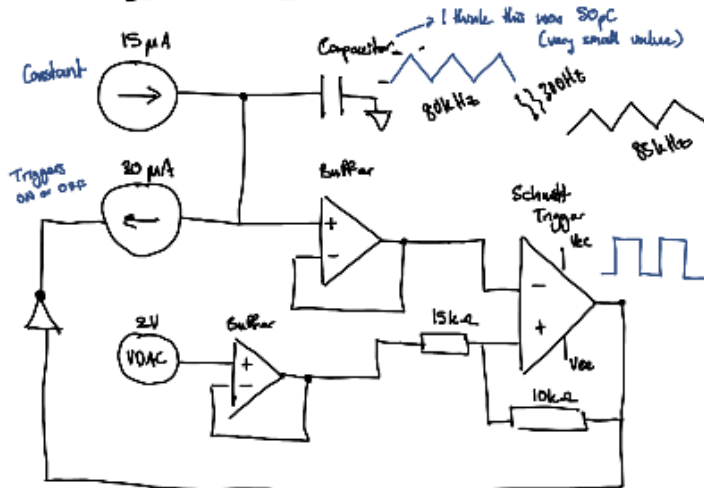Schmitt Trigger Design → Relaxation Oscillator




→ Observation: The schmitt was going at around 180kHz and any signal below it had no effect on it.

My thoughts... • What if we lower the frequency of the schmitt trigger? → can increase the capacitor

• What if we use a low pass filter type circuit?

↳ What happens if we put this into the design instead of a normal capacitor

Low Pass Filter

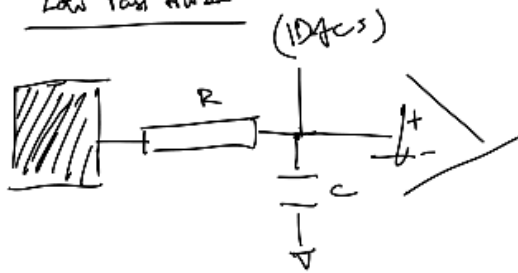


$$f_c = \frac{1}{2\pi RC} = 600\text{Hz}$$

$$RC = 0.000265$$

- IM - Intermodulation Frequencies

Relaxation Oscillator

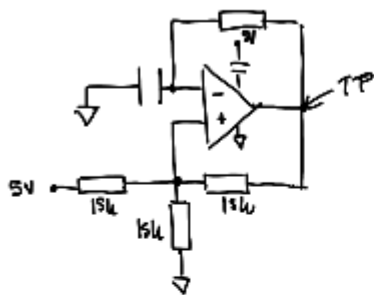

TL082 — Slew Rate = $13\text{V}/\mu\text{s}$



• How $2\text{V} \rightarrow \frac{2\text{V}}{13\text{V}/\mu\text{s}} = 0.38\mu\text{s}$


Say capacitor value is 10pF

$$\tau = RC$$

$$R = \frac{0.38\mu\text{s}}{10\text{pF}} = 38000\Omega$$






$$= 38\text{k}\Omega$$

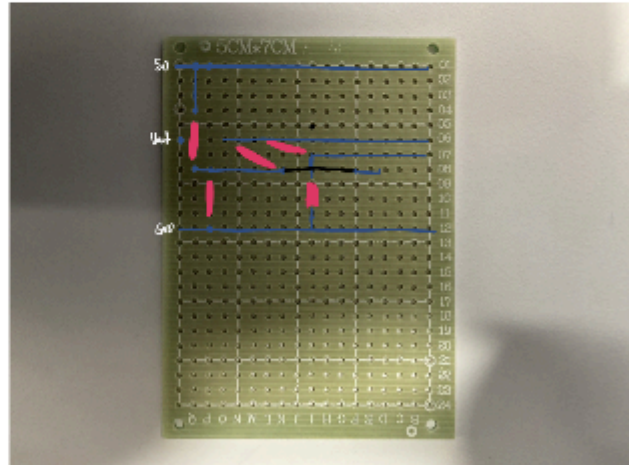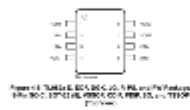

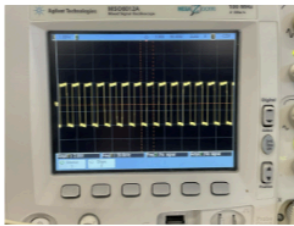

- 100 kHz

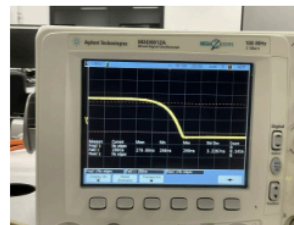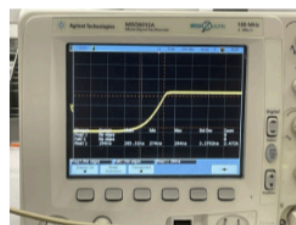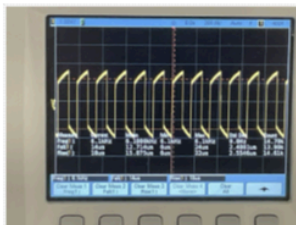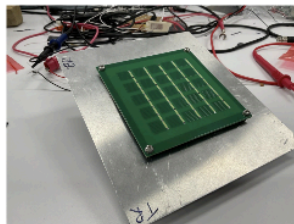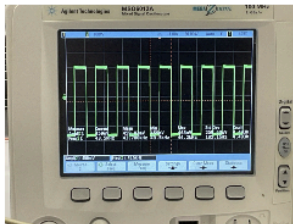on : rise time = 282.3 ns
! on : rise time = 282.3 ns




$$\tau = RC$$

$$0.000163743 = (10 \times 10^6)$$

$$C = 1.637 \times 10^{-11}$$

$$= 16.37 \text{ pF}$$

Charge Amplifier Circuit

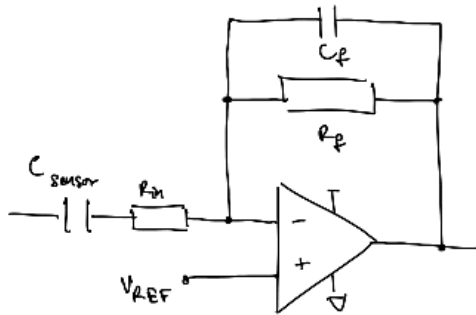

$$R_f = 10 \text{ M}\Omega$$

For low frequency cutoff at 10 Hz,

$$C_f = \frac{1}{2\pi R_f f_{\text{cutoff}}} = \frac{1}{2\pi \cdot (10 \text{ M}\Omega) \cdot (10 \text{ Hz})} = 1.59 \times 10^{-9} \text{ F}$$

For high frequency cutoff at 10 kHz, $\approx 1.5 \text{ nF}$ (standard value)

$$R_{in} = \frac{1}{2\pi C_{\text{sensor}} f_{\text{cutoff}}} = \frac{1}{2\pi \cdot (12 \times 10^{-12}) \cdot (10 \times 10^3)} = 1.326 \times 10^6 \Omega$$

$$\approx 1.2 \text{ M}\Omega \quad (\text{or } 1.5 \text{ M}\Omega)$$

expected output,

$$V_{\text{out}} = \frac{Q}{C_f}$$